

Baluns

How they work

How they are made

What is a balun?

- A Balun is special type of transformer that performs two functions:
 - Impedance transformation or matching (2:1, 4:1, 9:1 most common).
 - Balanced to unbalanced transformation.

The word balun is a contraction of “balanced to unbalance transformer.

Why do we need a balun?


- Baluns are important because many types of antennas (dipoles, yagis, loops) are balanced loads, which are fed with an unbalanced transmission line (coax).
- Baluns are for proper connection of parallel line to a transceiver with a 50 ohm unbalanced output
- The antenna’s radiation pattern changes if the currents in the driven element of a balanced antenna are not equal and opposite.
- With unbalanced RF currents in a coax.
 - Coax carries RF separately on inside and outside of the Shield.
 - The current on the outside shield can be high enough to cause burns if not grounded.
- Baluns prevent unwanted RF currents from flowing in the “third” conductor of a coaxial cable.

Balanced vs Unbalanced Transmission Lines

- A balanced transmission line is one whose currents are symmetric with respect to ground so that all current flows through the transmission line and the load and none through ground.
- Think about RF output as going “up” to the antenna, and unwanted “reflections” going down to the transmitter.
- Note that line balance depends on the current through the line, not the voltage across the line.

An example of a Balanced Line

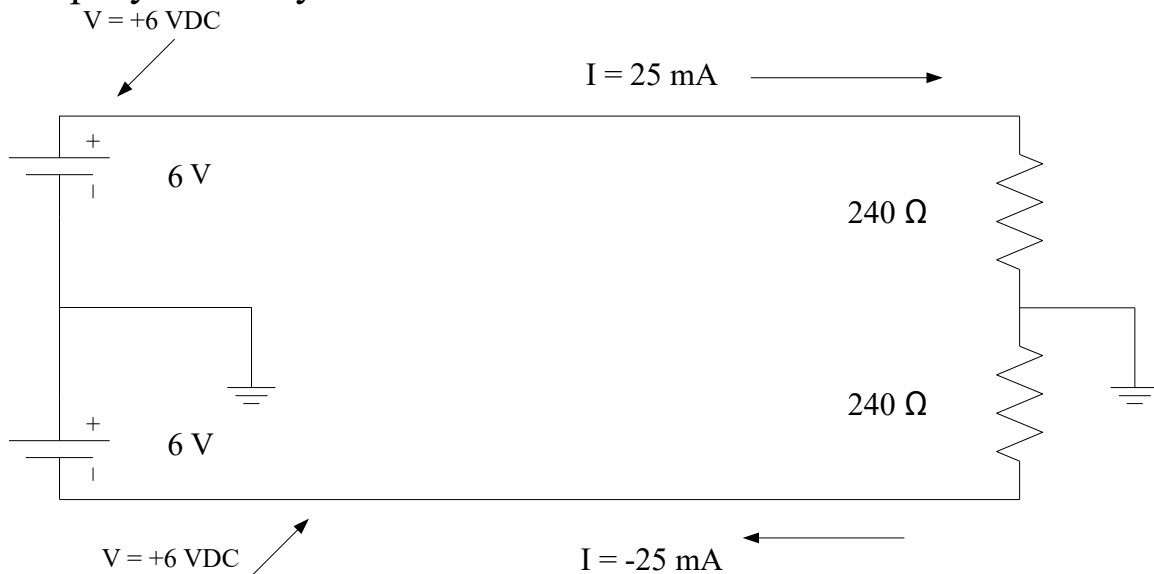
- Here is an example of a balanced line. DC rather than AC is used to simplify the analysis:



- Notice that the currents are equal and opposite and that the total current flowing through ground = $25\text{mA} - 25\text{mA} = 0$

Another Balanced Line Example


- Here is another example:

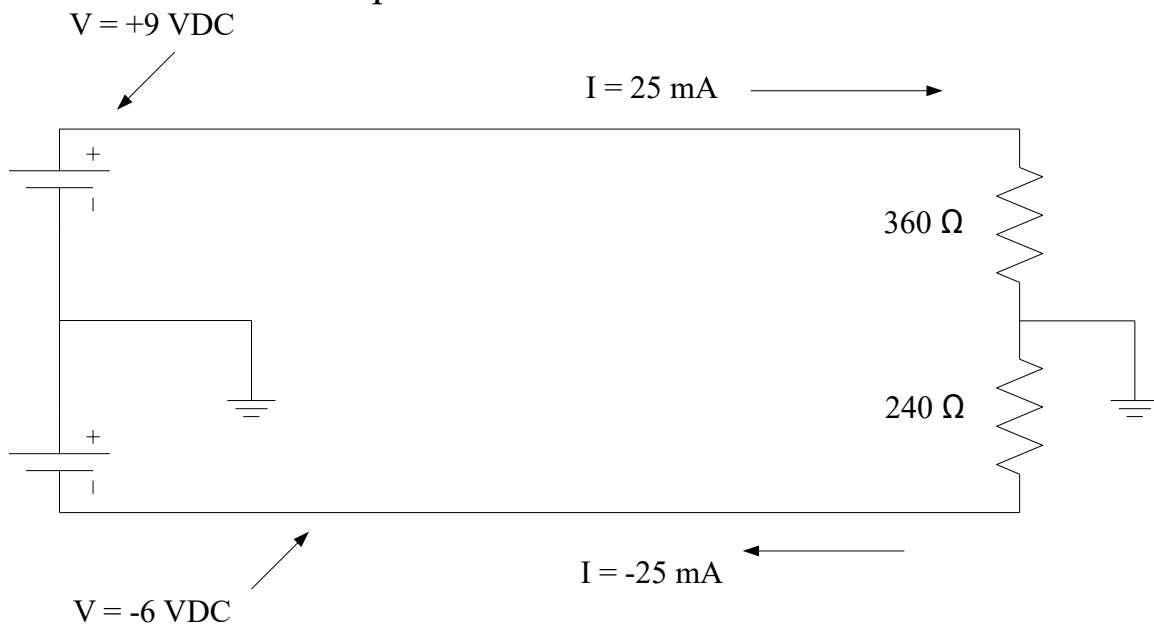

- Note that the total current flowing through ground is again 0
- Because the ground current is 0, the ground is not required

And Another Balanced Line Example

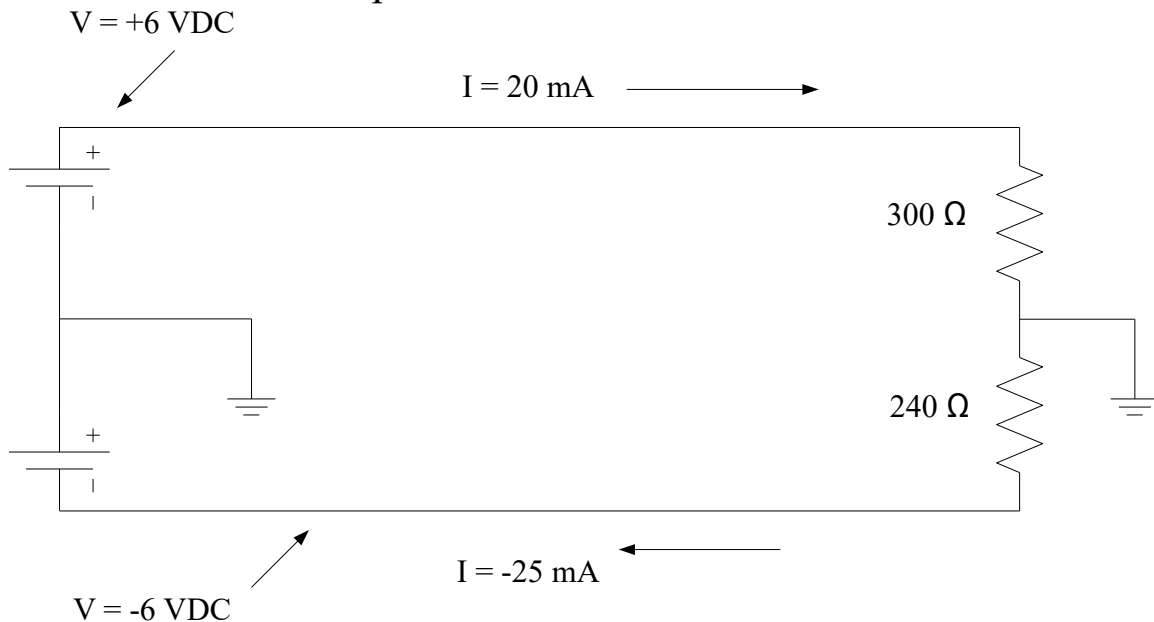- Here is another example. Is the line balanced?




- No – although the voltages are equal and opposite, the currents are not!

Voltage Baluns

- A Voltage Balun is one whose output voltages are equal and opposite (balanced with respect to ground).
- True balance occurs only if the balun's load is symmetric with respect to ground.
- Voltage baluns are easily constructed and commonly used in spite of their inability to provide true current balance.

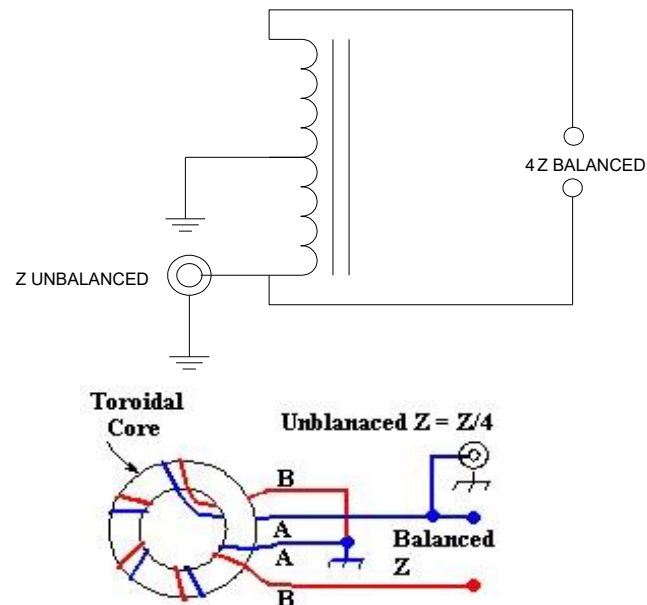
4:1 Voltage Balun

- This is the simplest voltage balun, consisting of two coils of wire connected as shown.
- The coils may use an air core or a ferrite core.
- Current flowing through the lower coil induces an equal and opposite voltage in the upper coil.
- The primary circuit contains N turns and the secondary $2N$, so the input impedance is $Z_L(N/2N)^2 = \frac{1}{4} Z_L$




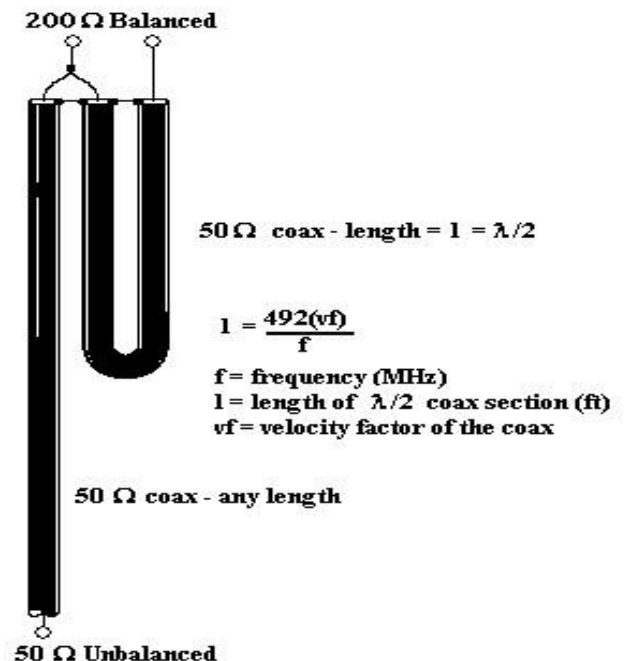
4:1 Transmission Line Voltage Balun

- This voltage balun is constructed solely from transmission line and requires no cores.
- Unlike the transformer type baluns, this balun may be used only over a narrow range of frequencies.
- The extra half wave section causes the voltage at its output to be equal and opposite to the voltage at the input



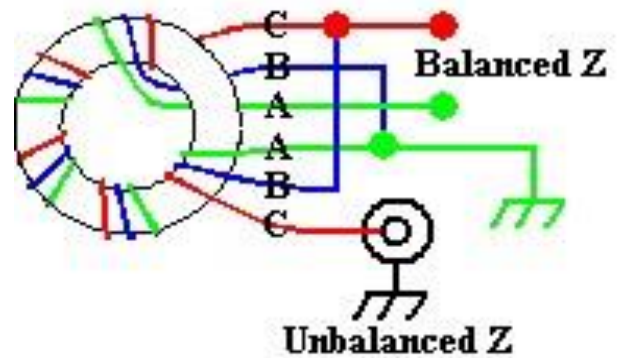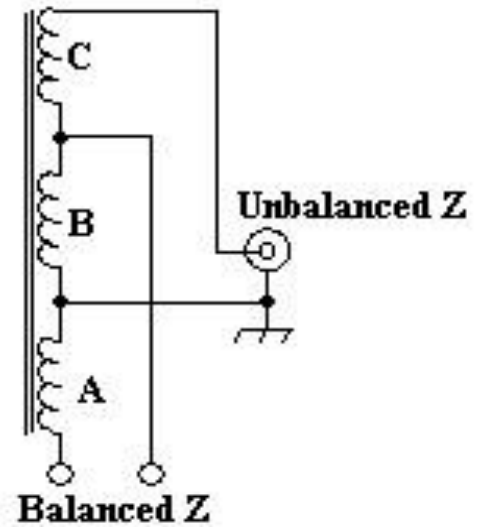1:1 Voltage Balun

- This voltage balun is similar to the 4:1, but uses 3 windings connected in series.
- The coils may use an air core or a ferrite core.
- Current flowing through the lower coil induces an equal and opposite voltage in the upper coil.
- The primary circuit contains N turns and the secondary
- N , so the input impedance is
- $Z_L(N/N)^2 = Z_L$





Current Baluns

- A Current Balun is one whose output currents are equal and opposite (balanced with respect to ground).
- With the exception of the 1:1 current balun, current baluns are more expensive to construct than voltage baluns and thus are less widely used.
- Current baluns may be made with RF transformers on ferrite cores or with lengths of transmission line.

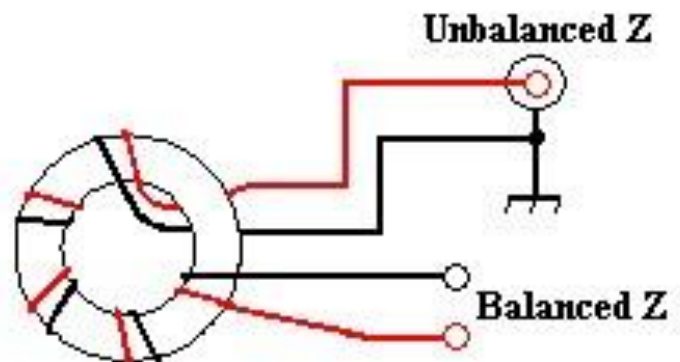
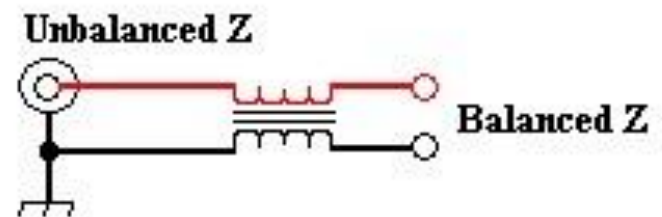
1:1 Current Balun

- This is the simplest current balun, consisting of two coils of wire connected as shown.
- The coils may use an air core or a ferrite core.
- Often a current balun is made by winding coaxial cable into a coil, with or without a ferrite core.
- The load impedance is not changed by the balun.
- The inductive reactance of the windings prevents common mode currents from flowing and ensures a balanced output
- The inductive reactance should be 10 times the load impedance at the lowest frequency of operation



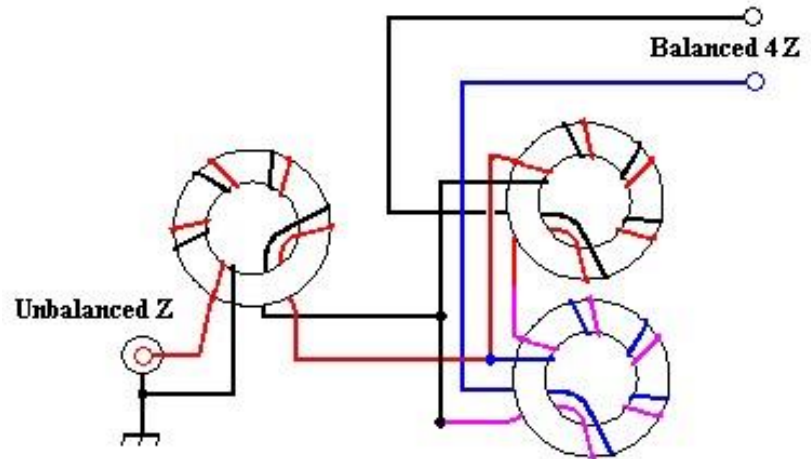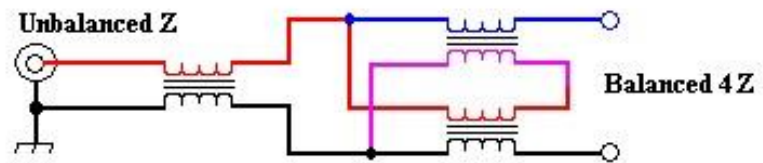4:1 Current Balun


- 6 windings on 3 cores are required to construct a 4:1 current balun.
- This balun consists of a 1:1 balun followed by a 4:1 balanced-to-balanced current transformer.
- The windings on the 1:1 balun should have at least an inductive reactance at least 10 times greater than the input impedance
- The windings on the 4:1 current transformer should have an inductive reactance at least 10 times greater than the output impedance (40 times Z_{in})



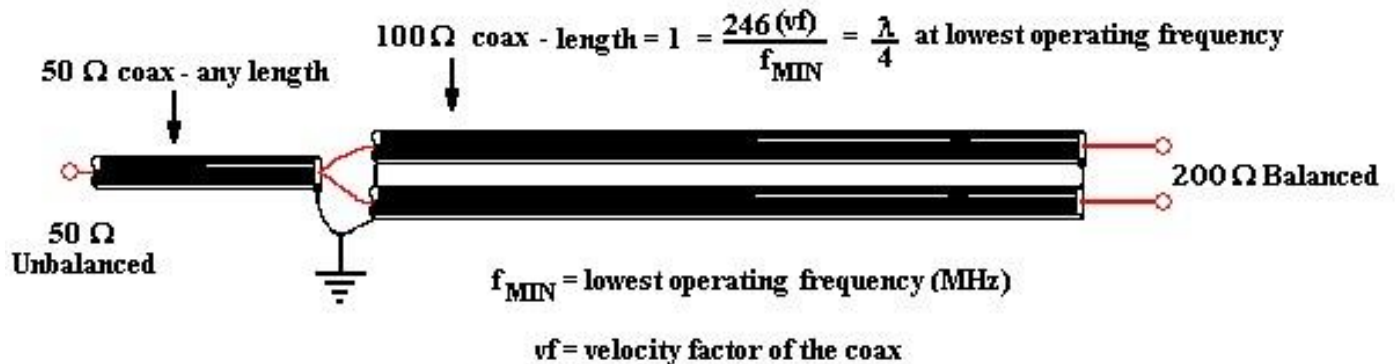4:1 transmission line current balun

- Only transmission line is needed to construct this current balun.
- The two lengths of transmission line that comprise the balun need to have a characteristic impedance of ~ 100 ohms. RG-62 ($Z = 95$ ohms) works very well.
- The length of the two sections of 100 ohm coax must be at least
- $\frac{1}{4}$ wavelength at the lowest frequency (approx. 47 feet at 3.5 MHz) and a this type of balun should work over a 8 to 1 frequency range.

- This type of balun is often used at higher frequencies where ferrite cores are lossy and short lengths of coax are required.



Notes about Balun Construction

- Transformer Baluns
 - Use solid wire, preferably enameled, for the windings.
 - For transmitting applications the wire should be #14 or larger
 - A 1.5 inch diameter ferrite/powdered iron core is sufficient for powers to 100 W. For QRO operation, use a 2.5 – 3 inch diameter core. Select the proper core material for the desired frequencies of operation
 - For HF baluns, 6 – 8 turns of wire around a toroidal core is sufficient. Air core baluns will need 10 – 20 turns
- Transmission line baluns
 - Coiling the coax sections improves common-mode rejection

FAQ's

- Do I really need a balun?
 - Not necessarily. If you feed a balanced antenna with unbalanced line and you don't want feed line radiation, use a balun!
- What kind of balun is best?
 - There is no best balun for all applications. The choice of balun depends on the type of antenna and the frequency range.
- Will you make a Balun for me?
 - No. However, I will be happy to show how to make your own.